

## Objective

- Familiarization with Input-Output I-V relationship of MOS transistors through measured characteristic data.
- To know practical values of device model parameters

## Components

- MOSFET
- Breadboard
- Resistors  $1k\Omega$
- Potentiometers  $10k\Omega$  and  $4k\Omega$  range
- Connecting wires

## Circuit Diagram

## Observation Table

### 0.1 $I_d$ versus $V_{DS}$ for $V_{gs}=7.8V$

| $V_{ds}(V)$ | $I_d(mA)$ |
|-------------|-----------|
| 1.53        | 12.02     |
| 1.78        | 12.01     |
| 1.97        | 11.83     |
| 2.14        | 11.54     |
| 2.24        | 11.29     |
| 2.31        | 11.05     |
| 2.36        | 10.88     |
| 2.45        | 10.54     |
| 2.55        | 10.13     |
| 2.63        | 9.78      |
| 2.7         | 9.38      |
| 2.77        | 9.04      |
| 2.81        | 8.86      |
| 2.87        | 8.57      |
| 2.91        | 8.19      |
| 2.98        | 7.81      |
| 3           | 7.67      |
| 3.06        | 7.27      |
| 3.11        | 6.98      |
| 3.17        | 6.55      |
| 3.22        | 6.14      |
| 3.3         | 5.64      |
| 3.4         | 4.99      |
| 3.43        | 4.57      |
| 3.51        | 4.11      |
| 3.61        | 3.83      |
| 3.59        | 3.46      |
| 3.64        | 2.94      |
| 3.69        | 2.6       |
| 3.74        | 2.08      |
| 3.78        | 1.7       |
| 3.85        | 1.22      |
| 3.94        | 0.99      |
| 4.1         | 0.8       |
| 4.88        | 0.54      |
| 5.86        | 0.41      |
| 6.3         | 0.38      |

## 0.2 $I_d$ versus $V_{DS}$ for $V_{gs}=9.7V$


| $V_{ds}(V)$ | $I_d(mA)$ |
|-------------|-----------|
| 0.0         | 12.06     |
| 1.33        | 12.07     |
| 1.74        | 12.06     |
| 2.27        | 11.58     |
| 2.31        | 11.4      |
| 2.42        | 11.13     |
| 2.54        | 10.86     |
| 2.67        | 10.48     |
| 2.83        | 9.95      |
| 3.03        | 9.15      |
| 3.19        | 8.5       |
| 3.27        | 8.07      |
| 3.45        | 7.39      |
| 3.56        | 6.86      |
| 3.68        | 6.18      |
| 3.8         | 5.53      |
| 3.81        | 5.37      |
| 3.86        | 5.1       |
| 3.94        | 4.78      |
| 4.07        | 3.89      |
| 4.11        | 3.63      |
| 4.19        | 3.13      |
| 4.29        | 2.48      |
| 4.35        | 2.16      |
| 4.57        | 1.29      |
| 4.73        | 1.1       |
| 4.93        | 0.96      |
| 5.42        | 0.78      |
| 5.69        | 0.72      |
| 6.15        | 0.64      |
| 7.63        | 0.5       |
| 10.14       | 0.4       |
| 11.2        | 0.36      |

### 0.3 Id versus $V_{GS}$ for $V_{ds}=6V$


| $V_{ds}(V)$ | $I_d(mA)$ |
|-------------|-----------|
| 1.74        | 12.04     |
| 1.88        | 11.9      |
| 2.0         | 11.63     |
| 2.14        | 11.13     |
| 2.23        | 10.69     |
| 2.28        | 10.38     |
| 2.37        | 9.79      |
| 2.44        | 9.29      |
| 2.51        | 8.71      |
| 2.58        | 8.13      |
| 2.61        | 7.87      |
| 2.65        | 7.52      |
| 2.68        | 7.18      |
| 2.74        | 6.55      |
| 2.78        | 6.17      |
| 2.82        | 5.69      |
| 2.86        | 5.27      |
| 2.88        | 5.0       |
| 2.91        | 4.68      |
| 2.95        | 4.17      |
| 2.98        | 3.78      |
| 3.03        | 3.25      |
| 3.08        | 2.52      |
| 3.12        | 2.09      |
| 3.36        | 0.58      |
| 4.17        | 0.31      |
| 4.45        | 0.28      |
| 4.83        | 0.25      |
| 5.61        | 0.2       |

## Plots


Plot of  $V_{OUT}$  vs  $V_{IN}$

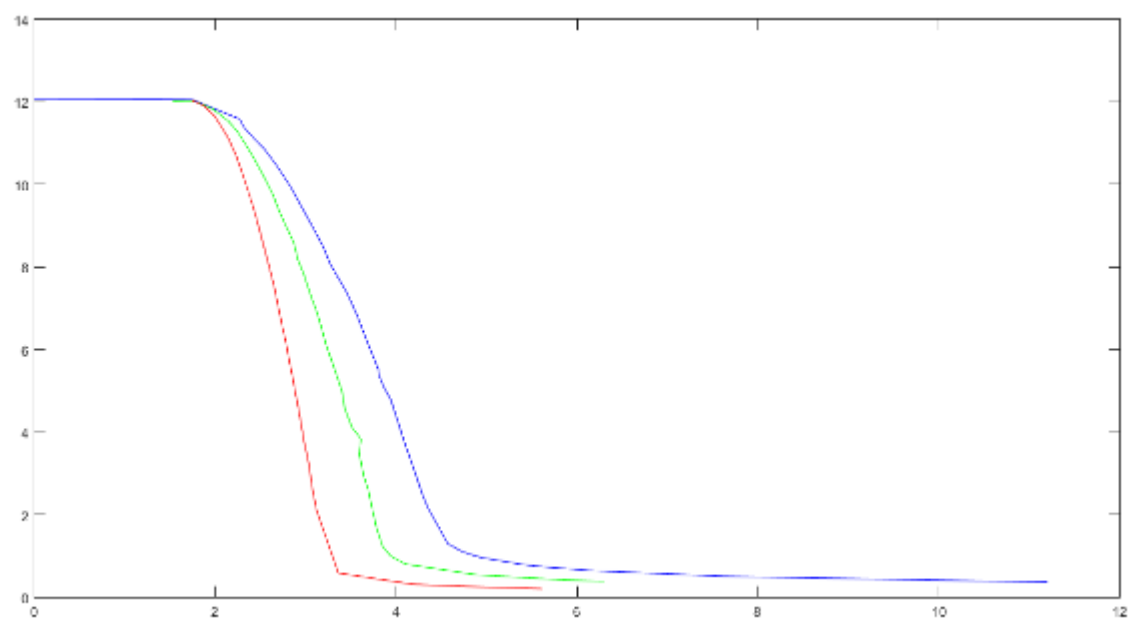


**Gain versus**

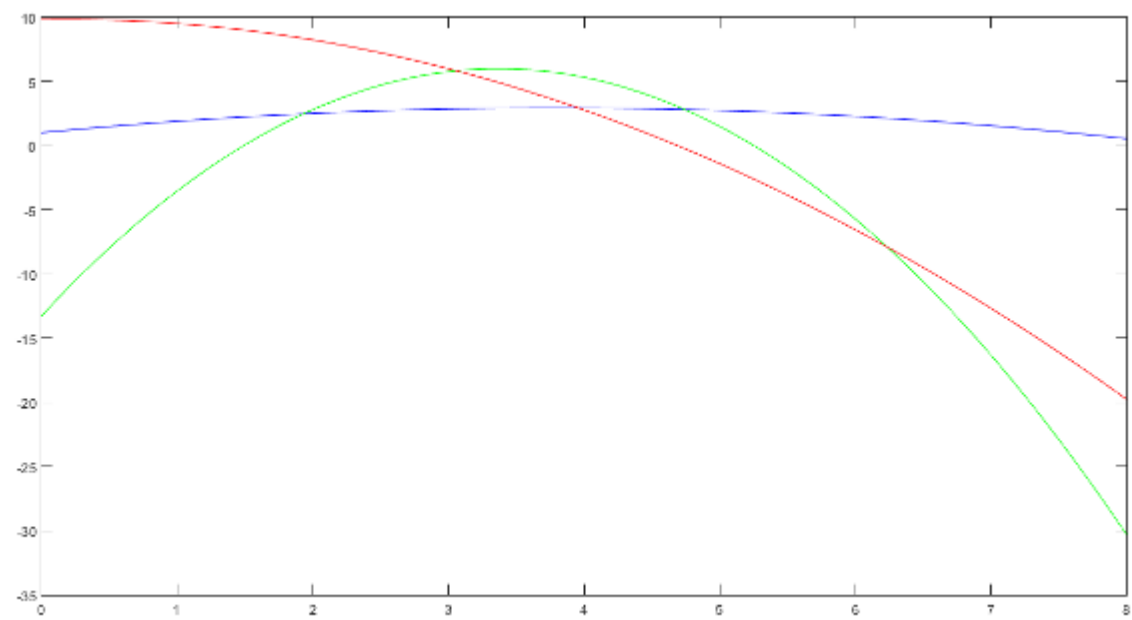


**Gain versus**

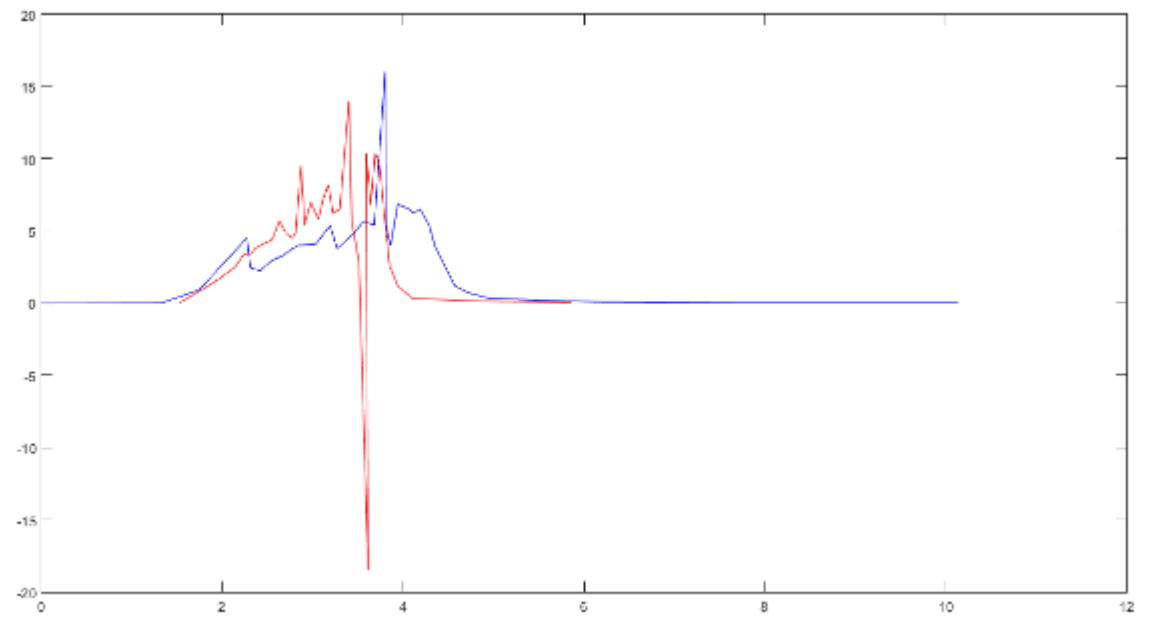


**Gain versus**

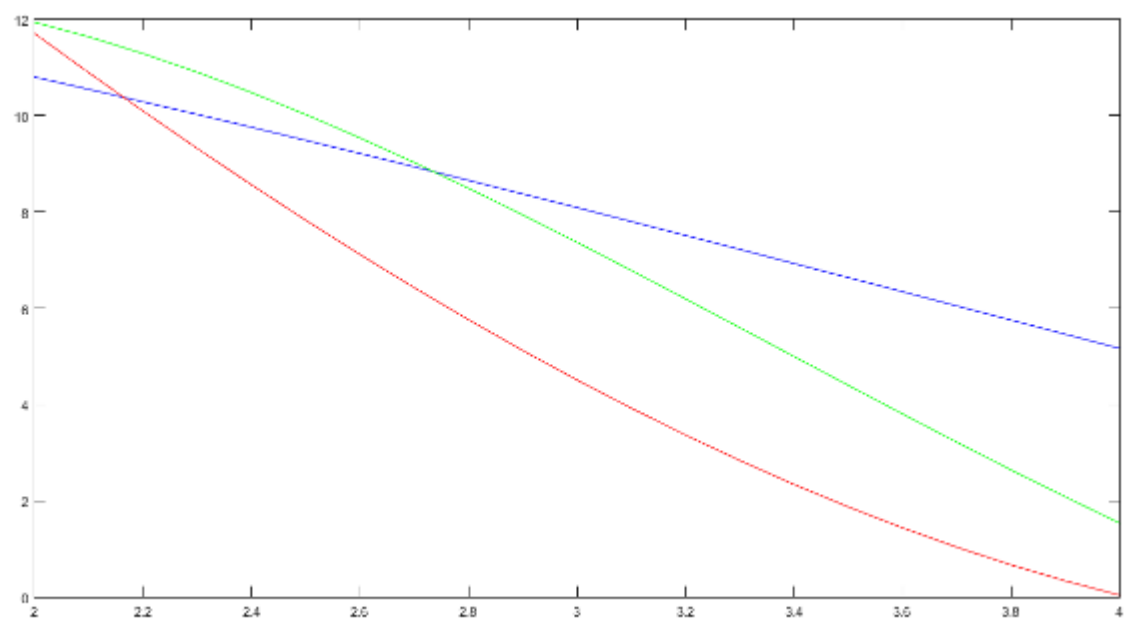

**Gain versus**

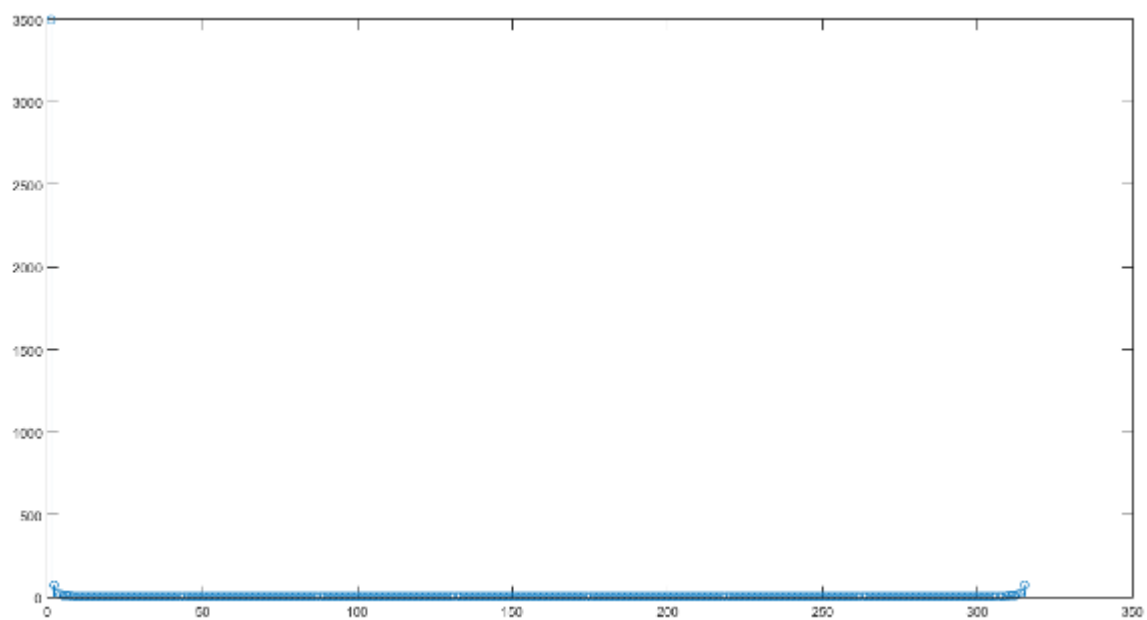


**Gain versus**

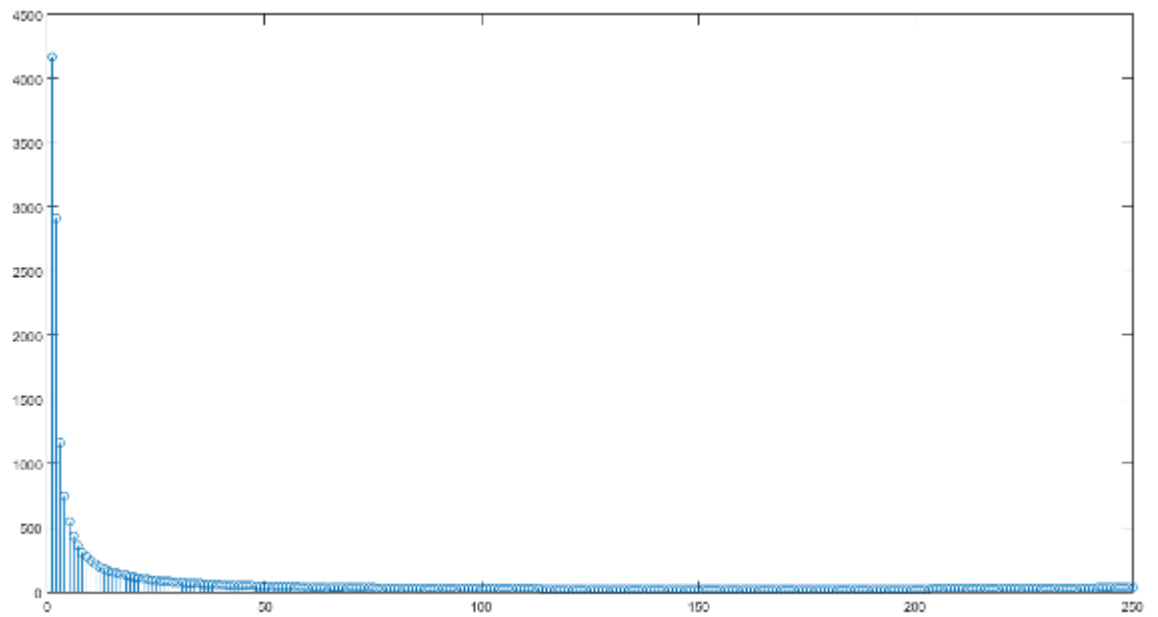

**Gain versus**



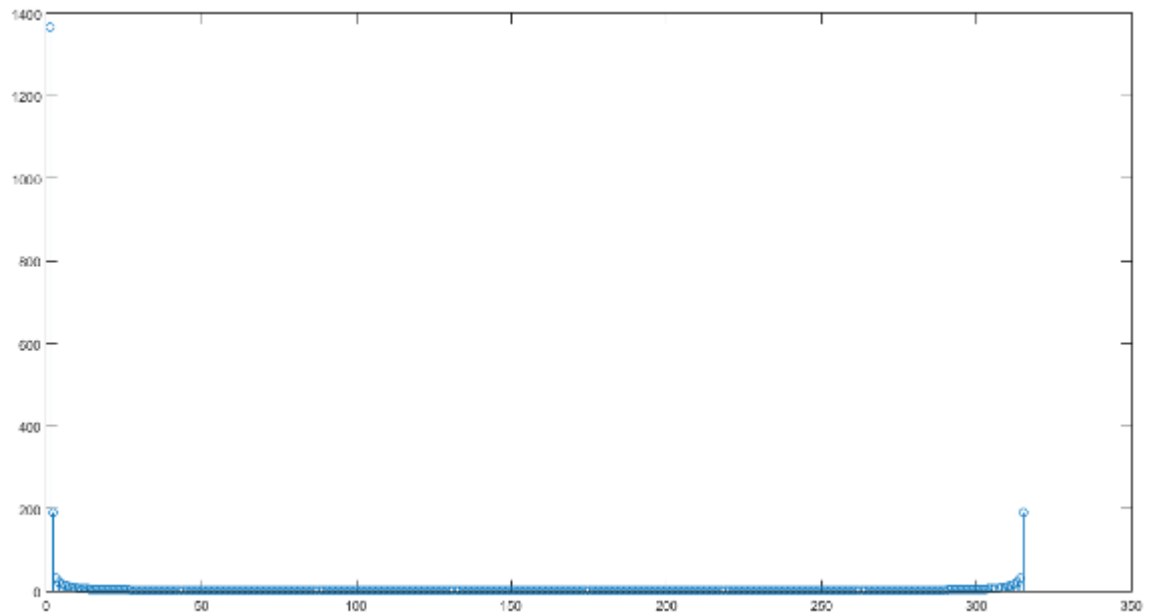

## Results

### THD values for

| $K_1^2$ | $\lambda(V^{-1})$     | $g_d(mS)$            |
|---------|-----------------------|----------------------|
| -9.59   | 0.104                 | 0.72                 |
| -220.49 | $4.5 \times 10^{-3}$  | $9.4 \times 10^{-3}$ |
| -358.19 | $2.79 \times 10^{-3}$ | 0.017                |

### Large signal parameters from $I_d$ vs $V_{ds}$ plot

| $V_{th}(V)$ | k    | $g_m(m\Omega)$ |
|-------------|------|----------------|
| 4.14        | 2.25 | 2.25           |

## Discussion

### 14EC10043

From the characteristics we could observe that in the output characteristics as  $V_{ds}$  increases the  $I_d$  increases up to the transition point.

After the transition the curve didn't remain perfectly horizontal as expected and this is due to the channel width modulation effect.

While measuring  $I_d$  with respect to  $V_{gs}$  we must keep  $V_{ds}$  constant in our experiment we must adjust the value of drain resistance to keep  $V_{ds}$  constant it was found roughly constant

### **14EC10049**

In the graph  $i_d$  vs  $V_{ds}$  the nonzero slope even after in the saturation region gives the value of  $V_a$  which is a negative value this non zero slope is due to the channel effect this is also known as channel length modulation

The additional resistance kept in the circuit other than the potentiometer is to avoid burning of transistor due to high drain current.

While do  $i_d$  vs  $V_{gs}$  we have to measure the value at constant  $V_{ds}$  but in our experiment we can observe  $V_{ds}$  decreasing this can be adjusted every time as precise as possible as the potentiometer range is not wide we can adjust upto some extent only. Chat Conversation End